 


1) Design and simulate BCD to Excess 3 converter using Verilog programming.



$$w = A + BC + BD$$

$$x = B'C + B'D + BC'D'$$

$$y = CD + C'D'$$

$$z = D'$$

BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

```

module BCEtoE3(a,b,c,d,w,x,y,z);
input a,b,c,d;
output w,x,y,z;
assign w = (a | (b & c) | (b & d));
assign x = (((~b) & c) | ((~b) & d) | (b & (~c) & (~d)));
assign y = ((c & d) | ((~c) & (~d)));
assign z = ~d;
endmodule

```

2) Design and simulate the Boolean function, $F = X'Y'Z + X'YZ + XY'$ using Verilog programming.

```

module boolxyz(x,y,z,f);
input x,y,z;
output f;
assign f = (((~x) & (~y) & z) | ((~x) & (y) & z) | ((x) & (~y)));
endmodule

```

3) Design and simulate the Boolean function, $F = B'D' + B'C' + A'C'D$ using Verilog programming.

```

module boolbd(a,b,c,d,f);
input a,b,c,d;
output f;
assign f = (((~b) & (~d)) | ((~b) & (~c)) | ((~a) & (~c) & (d)));
endmodule

```

4) Design and simulate the Boolean function, $F = (A' + B') \cdot (C' + D') \cdot (B' + D)$ using Verilog programming.

```

module boolab(a,b,c,d,f);
input a,b,c,d;
output f;
assign f = (((~a) | (~b)) & ((~c) | (~d)) & ((~b) | (d)));
endmodule

```


5) Design an OR gate by using a NAND gate and simulate using Verilog programming.

We first compliment the inputs A and B. Using de morgan's law $(A'B')' = A + B$.

```

module or_nand(a,b,y);
input a,b;
output y;
wire p,q;
nand(p,a,a);
nand(q,b,b);
nand(y,p,q);
endmodule


```

 

 6) Design an AND gate by using a NOR gate and simulate using Verilog programming.

We first compliment the inputs A and B. Then we perform the NOR operation on these complemented inputs. We get $(A'+B')'$.

Using demorgan's law: $(A'+B')' = A \cdot B$




A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

```
module and_nor(a,b,y);
input a,b;
output y;
wire p,q;
nor(p,a,a);
nor(q,b,b);
nor(y,p,q);
endmodule
```

7) Design an XOR gate by using a NAND gate and simulate using Verilog programming.

 
1. $P = A \text{ nand } B = (AB)'$
2. $Q = A \text{ nand } (AB)' = (A(AB)')'$
3. $R = B \text{ nand } (AB)' = (B(AB)')'$
4. $Y = (A(AB)')' \text{ nand } (B(AB)')' = ((A(AB)')') \cdot (B(AB)')')'$



```
module xor_nand(a,b,y);
input a,b;
output y;
wire p,q,r;
nand(p,a,b);
nand(q,a,p);
nand(r,b,p);
nand(y,q,r);
endmodule
```


8) Design an XOR gate by using a NOR gate and simulate using Verilog programming.

 1. $P = A \text{ nor } B = (A+B)'$
2. $Q = A \text{ nor } (A+B)' = (A+(A+B)')'$
3. $R = B \text{ nor } (A+B)' = (B+(A+B)')'$
4. $S = Q \text{ nor } R = ((A+(A+B)')' + (B+(A+B)')')' = ((A'.B)+(A.B'))'$
5. $Y = S \text{ nor } S = (A'.B)+(A.B')$




```
module xor_nor(a,b,y);
input a,b;
output y;
wire p,q,r,s;
nor(p,a,b);
nor(q,a,p);
nor(r,b,p);
nor(s,q,r);
nor(y,s,s);
endmodule
```

 9) Design a circuit to prove DeMorgan's first theorem and simulate using Verilog programming.




```
module demorgan_one(a,b,y_nand,y_or);
input a,b;
output y_nand,y_or;
nand(y_nand,a,b);
wire p,q;
not(p,a);
not(q,b);
or(y_or,p,q);
endmodule
```

 10) Design a circuit to prove DeMorgan's second theorem and simulate using Verilog programming.



```
module demorgan_two(a,b,y_nor,y_and);
input a,b;
output y_nor,y_and;
nor(y_nor,a,b);
wire p,q;
not(p,a);
not(q,b);
and(y_and,p,q);
endmodule
```

 
11) Design a combinational circuit to perform addition of two bits and simulate using Verilog programming.



INPUTS		OUTPUTS	
a	b	Sum ($a \oplus b$)	Carry (a.b)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

```
module HalfAdder(a,b,sum,carry);
input a,b;
output sum,carry;
xor(sum,a,b);
and(carry,a,b);
endmodule
```

 12) Design a combinational circuit to perform addition of three bits and simulate using Verilog programming.




```

module FullAdder(a,b,c,sum,carry);
input a,b,c;
output sum,carry;
assign sum = ((a^b)^c);
assign carry = ((a&b) | (b&c) | (c&a));
endmodule

```

 13) Design a combinational circuit to perform subtraction of two bits and simulate using Verilog programming.




```

module HalfSubtractor(A,B,Diff,Borrow);
input A,B;
output Diff,Borrow;
wire x;
xor (Diff, A,B);
not(x,A);
and(Borrow,x,B);
endmodule

```

 14) Design a combinational circuit to perform subtraction of three bits and simulate using Verilog programming.




```


module FullSubtractor(A,B,C,Diff,Borrow);
input A,B,C;
output Diff,Borrow;
wire p;
assign Diff = ((A^B)^C);
not(p,A);
assign Borrow = ((p&B) | (p&C) | (B&C));
endmodule

```

 
15) Obtain the Boolean expression for F1, F2 and simulate the output using Verilog programming.



 16) Obtain the Boolean expression for F, G and simulate the output using Verilog programming.



 17) Design and simulate 4-bit parity generator using Verilog programming.



4-bit received message				Parity error check C_p
A	B	C	P	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

```

module parity(x,y,z,p,c);
input x,y,z,p;
output c;
wire a,b;
xor(a,x,y);
xor(b,z,p);
xor(c,a,b);
endmodule


```

18) Implement the function $F(A, B, C) = \sum m(1,3,5,6)$ by 4:1 multiplexer and simulate using Verilog programming.

19) Implement the function $F(p, q, r, s) = \sum m(0,1,3,4,8,9,15)$ by 8:1 multiplexer and simulate using Verilog programming.

20) Design a 1:4 De-multiplexer and simulate using Verilog programming.

S1	S0	D	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	0	0
1	1	1	1	0	0	0

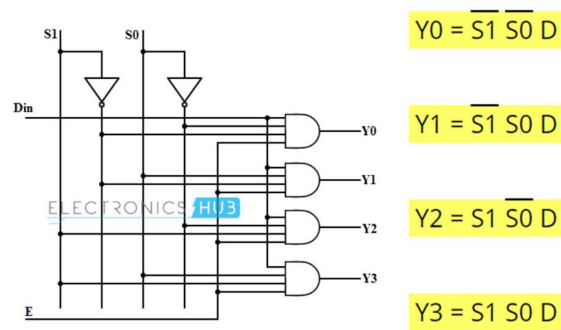


```

module demux(I,S0,S1,Y0,Y1,Y2,Y3);
input I,S0,S1;
output Y0,Y1,Y2,Y3;
wire S0C,S1C;
not(S0C,S0);
not(S1C,S1);
and(Y0,I,S0C,S1C);
and(Y1,I,S0C,S1);
and(Y2,I,S0,S1C);
and(Y3,I,S0,S1);
endmodule

```

21) Design a 1:8 De-multiplexers and simulate using Verilog programming.

S2	S1	S0	Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0	0	0	D
0	0	1	0	0	0	0	0	0	D	0
0	1	0	0	0	0	0	0	D	0	0
0	1	1	0	0	0	0	D	0	0	0
1	0	0	0	0	0	D	0	0	0	0
1	0	1	0	0	D	0	0	0	0	0
1	1	0	0	D	0	0	0	0	0	0
1	1	1	D	0	0	0	0	0	0	0

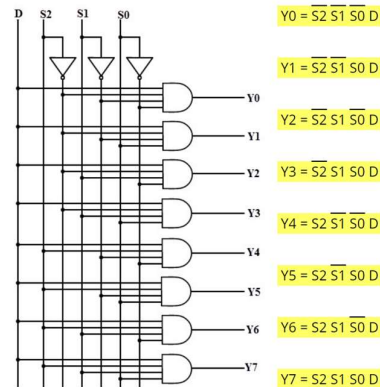

```

module demul_eight(D,S0,S1,S2,Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);
input D,S0,S1,S2;
output Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7;
wire S0C,S1C,S2C;
not(S0C,S0);
not(S1C,S1);
not(S2C,S2);
and(Y0,I,S2C,S1C,S0C);
and(Y1,I,S2C,S1C,S0);
and(Y2,I,S2C,S1,S0C);
and(Y3,I,S2C,S1,S0);
and(Y4,I,S2,S1C,S0C);
and(Y5,I,S2,S1C,S0);
and(Y6,I,S2,S1,S0C);
and(Y7,I,S2,S1,S0);
endmodule

```


22) Design an 8:3 Decoder and simulate using Verilog programming.

Enable	INPUTS			Outputs							
E	A ₂	A ₁	A ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

$$D_0 = \bar{A}\bar{B}\bar{C}, \quad D_1 = \bar{A}\bar{B}C, \quad D_2 = \bar{A}B\bar{C},$$

$$D_3 = \bar{A}BC, \quad D_4 = A\bar{B}\bar{C}, \quad D_5 = A\bar{B}C,$$

$$D_6 = AB\bar{C}, \quad D_7 = ABC$$

 


```

module decode(a,b,c,d0,d1,d2,d3,d4,d5,d6,d7);
input a,b,c;
output d0,d1,d2,d3,d4,d5,d6,d7;
assign d0 = (~a&~b&~c);
assign d1 = (~a&~b&c);
assign d2 = (~a&b&~c);
assign d3 = (~a&b&c);
assign d4 = (a&~b&~c);
assign d5 = (a&~b&c);
assign d6 = (a&b&~c);
assign d7 = (a&b&c);
endmodule

```

23) Design a 4:2 Decoder and simulate using Verilog programming.

Enable	Inputs		Outputs			
E	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

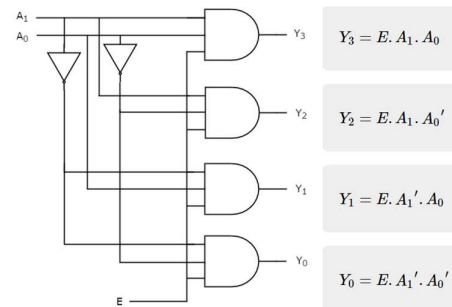

```

module decode(a,b,d0,d1,d2,d3);
input a,b;
output d0,d1,d2,d3;
assign d0 = (~a&~b);
assign d1 = (~a&b);
assign d2 = (a&~b);
assign d3 = (a&b);
endmodule


```

24) Design a 2:4 Encoder and simulate using Verilog programming.

INPUTS				OUTPUTS	
Y3	Y2	Y1	Y0	A1	A0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

$$A1 = Y3 + Y2$$


$$A0 = Y3 + Y1$$

 

```
module encod(d0,d1,d2,d3,a,b);
input d0,d1,d2,d3;
output a,b;
or(a,d3,d2);
or(b,d3,d1);
endmodule
```

25) Design a 3:8 Encoder and simulate using Verilog programming.

INPUTS								OUTPUTS		
Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

 

```
module encod(d0,d1,d2,d3,d4,d5,d6,d7,a,b,c);
input d0,d1,d2,d3,d4,d5,d6,d7;
output a,b,c;
or(a,d4,d5,d6,d7);
or(b,d2,d3,d6,d7);
or(c,d1,d3,d5,d7);
endmodule
```

26) Design a mod 5 counter and simulate using Verilog programming.


```
module sr(clock,up);
input clock;
output reg[0:3]up;
always @(posedge clock)
begin
up=up+1;
if(up==5)
up=0;
end
endmodule
```


27) Design a Decade counter and simulate using Verilog programming.

```

module sr(clock,up);
input clock;
output reg[0:3]up;
always @(posedge clock)
begin
up=up+1;
if (up==10)
up=0;
end
endmodule

```

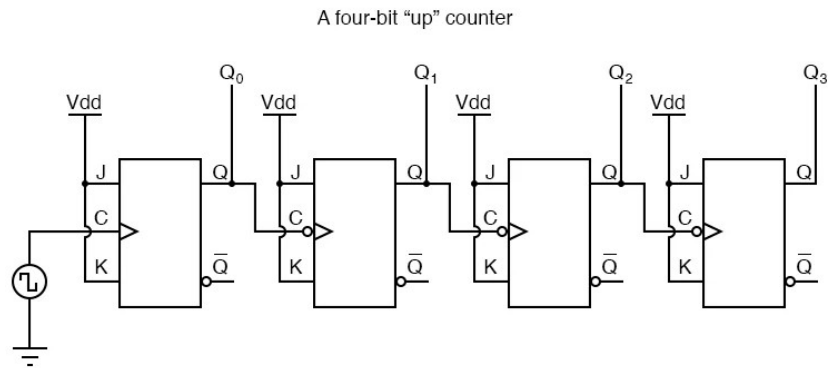


28) Design a clocked flip flop for the given truth table and simulate using Verilog programming. – SR Flip Flop

Input		Output		State
0	0	1	1	Invalid
0	1	0	1	Q' is set as 1
1	0	1	0	Q is set as 1
1	1	1	0	No change

```

module sr(s,r,clock,q,qbar);
input s,r,clock;
output q,qbar;
wire x,y;
nand(x,s,clock);
nand(y,r,clock);
nand(q,x,qbar);
nand(qbar,y,q);
endmodule

```

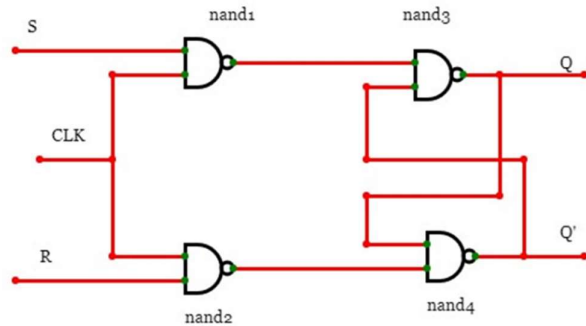


29) Design a clocked flip flop for the given truth table and simulate using Verilog programming. – JK Flip Flop

Input		Output		State
0	0	1	1	No change
0	0	1	1	No change
0	1	0	1	Q' is set as 1
1	0	1	0	Q is set as 1
1	1	1	0	Toggle
1	1	0	1	Toggle

```

module jkflp(J,K,Clock,Q,Qbar);
input J,Clock,K;
output Q,Qbar;
wire S,R;
nand (S,J,Clock,Qbar);
nand (R,K,Clock,Q);
nand (Q,S,Qbar);
nand (Qbar,R,Q);
endmodule

```

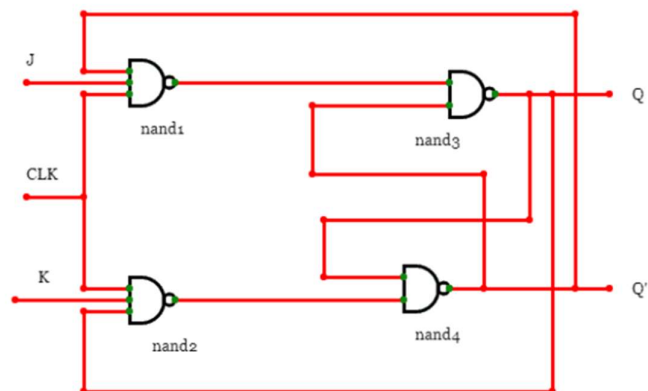


30) Design a clocked flip flop for the given truth table and simulate using Verilog programming. – D Flip Flop

Clk	Input	Output		State
0	0	1	1	No change
0	1	1	1	No change
1	0	0	1	Q' is set as 1
1	1	1	0	Q is set as 1

```

module dflp(D,Clock,Q,Qbar);
input D,Clock;
output Q,Qbar;
assign Dbar = ~D;
wire X,Y;
nand (X,D,Clock);
nand (Y,Dbar,Clock);
nand (Q,X,Qbar);
nand (Qbar,Y,Q);
endmodule

```

 

31) Design a clocked flip flop for the given truth table and simulate using Verilog programming. – T Flip Flop

Clk	Input	Output		State
0	0	1	1	No change
0	1	1	1	No change
1	0	1	1	No change
1	1	1	0	Complement

```

module tflp(T,Clock,Q,Qbar);
input T,Clock;
output Q,Qbar;
wire A,B;
nand (A,T,Clock,Qbar);
nand (B,T,Clock,Q);
nand (Q,A,Qbar);
nand (Qbar,B,Q);
endmodule

```

